

2 0 1 3

(1st Semester)

ELECTRONICS

FIRST PAPER

(Electronic Measuring Instruments and Circuit Analysis)

(PART : A—OBJECTIVE)

(Marks : 20)

Answer **all questions**

SECTION—I

(Marks : 5)

Each question carries 1 mark

Tick (✓) the correct answer in the brackets provided :

1. No colour coding in a resistor indicates the tolerance of

(a) 5% ()

(b) 10% ()

(c) 20% ()

(d) 25% ()

(2)

2. A device that converts energy in one form to energy in another form is

(a) transformer ()

(b) transducer ()

(c) thermocouple ()

(d) thermistor ()

3. Unit of impedance is in

(a) ohm ()

(b) henry ()

(c) mho ()

(d) farad ()

4. Kirchhoff's voltage law (KVL) is concerned with

(a) IR drops ()


(b) battery EMF's ()

(c) junction voltage ()

(d) Both (a) and (b) ()

(3)

5. Total resistance of the network

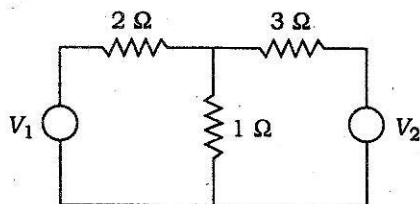

is

(a) $6\ \text{ohm}$ ()

(b) $\frac{16}{5}\ \text{ohm}$ ()

(c) $\frac{11}{3}\ \text{ohm}$ ()

(d) $\frac{11}{4}\ \text{ohm}$ ()

(4)

SECTION—II

(Marks : 15)

Each question carries 3 marks

1. Briefly explain the sharpness of resonance circuit.


(5)

2. A power transformer has 200 primary turns and 800 secondary turns. If the primary voltage is 230 volts and full-load primary current is 20 amperes, find the secondary voltage and current.

3. Describe how a bandpass filter works.


(7)

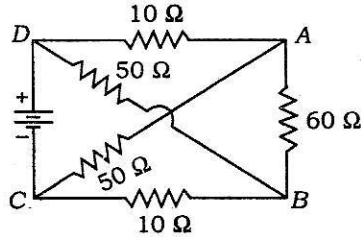4. Find the current in the branch AB of the network using nodal analysis for the circuit



(8)

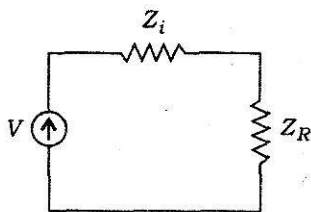5. A generating device has an impedance Z_i and is connected to a load by a line of Z_R . At what load will maximum power transfer received by the load when adjusted for maximum power?



$$Z_i = 1.5 - j1; Z_e = 1.5 - j4; V = 30\text{V}$$

2 0 1 3

(1st Semester)

ELECTRONICS

FIRST PAPER

**(Electronic Measuring Instruments and
Circuit Analysis)**

Full Marks : 55

Time : 2 hours

(PART : B—DESCRIPTIVE)

(Marks : 35)

*The figures in the margin indicate full marks
for the questions*

UNIT—I

1. (a) What are the different types of inductors? 2

**(b) Define inductance and derive an
expression for mutual inductance of two
coils. 2+3=5**

Or

**(a) Describe the construction of ceramic
capacitor. Why is a ceramic capacitor
preferred over a mica or a paper
capacitor? 2+2=4**

(2)

- (b) Compare among wire-wound, carbon-film and carbon-composition resistors. 3

UNIT—II

2. Describe the principle of working of cathode-ray oscilloscope. 7

Or

- (a) Can you operate a transformer on a constant DC voltage? Describe how an auto-voltage transformer works. 1+4=5
(b) What is a multimeter? Define the sensitivity of a multimeter. 1+1=2

UNIT—III

3. Derive an expression of alternating current through a series LRC circuit. 7

Or

What do you mean by j -operator? Derive the impedance of an RC circuit. 2+5=7

UNIT—IV

4. (a) What do you mean by 'node' and 'loop'? 2
(b) What is loop matrix? How will you express the complete loop matrix having 3 loops and 4 branches? 2+3=5

(3)

Or

- (a) How will you convert a current source into a voltage source? 3
(b) State and explain the ladder method of network analysis. 4

UNIT—V

5. (a) State Thevenin's theorem and prove it in case of a two-terminal network. 4
(b) Show that the Norton's equivalent circuit can be found from the Thevenin's equivalent circuit. 3

Or

- (a) State the maximum power transfer theorem and give its applications. 3+1=4
(b) Explain the superposition theorem. 3
