

**2 0 1 5**

( 1st Semester )

**ELECTRONICS**

Paper No : EL-101

( **Electronic Measuring Instruments and Circuit Analysis** )

( PART : A—OBJECTIVE )

( Marks : 20 )

Answer **all** questions

**SECTION—I**

( Marks : 5 )

*Each question carries 1 mark*

Tick ( ✓ ) the correct answer in the brackets provided :

1. The phase difference between voltage and current in the circuit containing a pure resistor is

(a)  $90^\circ$  ( )

(b)  $180^\circ$  ( )

(c)  $0^\circ$  ( )

(d)  $360^\circ$  ( )

( 2 )

2. The capacitor used in the filter circuits in order to remove the a.c. ripple from the power supply is

(a) electrolytic capacitor ( )

(b) paper capacitor ( )

(c) ceramic capacitor ( )

(d) mica capacitor ( )

3. The main purpose of laminating a transformer core is to decrease its

(a) electrical resistance ( )

(b) reluctance ( )

(c) eddy current loss ( )

(d) hysteresis loss ( )

4. What is the equivalent voltage for a current source of 5 A in series with  $2\ \Omega$  resistance?

(a) 10 V ( )

(b) 2.5 V ( )

(c) 7 V ( )

(d) 3 V ( )

5. To get the Thevenin's voltage, you have to

(a) short circuit the load resistor ( )

(b) open the load resistor ( )

(c) short circuit the voltage source ( )

(d) open the voltage source ( )

( 4 )

SECTION—II

( Marks : 15 )

Answer *any* **five** questions

*Each question carries 3 marks*

1. Define phasor and phasor diagram.

( 5 )

2. Define transducer. What is the difference between passive and active transducers?

( 6 )

3. What are acceptor and rejector circuits? Why are they named so?

4. Explain briefly ideal and practical current source.


5. What are the merits and demerits of a multimeter?



6. List down some uses of filter circuits.

( 10 )

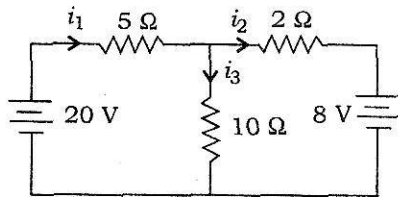7. For the given circuit, find  $i_1$ ,  $i_2$  and  $i_3$  using Nodal analysis :



8. What do you mean by varactor? What is the difference between abrupt-junction and hyper-abrupt junction of varactor?

\*\*\*

**2015**

**( 1st Semester )**

**ELECTRONICS**

**Paper No : EL-101**

**( Electronic Measuring Instruments and  
Circuit Analysis )**

*Full Marks : 55*

*Time : 2½ hours*

**( PART : B—DESCRIPTIVE )**

**( Marks : 35 )**

*The figures in the margin indicate full marks  
for the questions*

1. (a) What do you mean by power rating of a resistor? Describe briefly the preparation of wire-wound resistor and carbon composition resistor. 1+2+2=5
- (b) A varactor diode has a capacitance of 16 pF when the reverse bias voltage applied across it is 3 V. Determine the capacitance if the diode bias voltage is 6 V. 2

Or

(a) What do you mean by voltage rating of capacitors? Describe the preparation and uses of electrolytic capacitors. 1+3=4

(b) Define inductance. What are the different types of inductors? 1+2=3

2. Describe the principle of working of cathode-ray oscilloscope. 7

Or

Describe in detail the construction and working principle of a transformer. Why is laminated core necessary in a transformer? 2+3+2=7

3. (a) Explain how bandpass filter works. 3

(b) What is quality factor of a resonant circuit? Derive the expression for quality factor of a series resonant circuit. 1+3=4

Or

(a) A series resonance circuit has  $L = 1.01 \text{ H}$ ,  $C = 20 \mu\text{F}$  and  $R = 70 \Omega$  to which an e.m.f. of  $100 \text{ V}$  (r.m.s.) is applied. At what frequency of the applied e.m.f. will it resonate with maximum response? 4

(b) Derive the voltage and current relations in a.c. circuit containing  $R$  and  $C$ . 3


4. (a) Differentiate between the following :  $2 \times 2 = 4$

(i) Linear and Non-linear elements

(ii) Unilateral and Bilateral elements

(b) For the given circuit, determine the currents indicated using current divider formula :

3

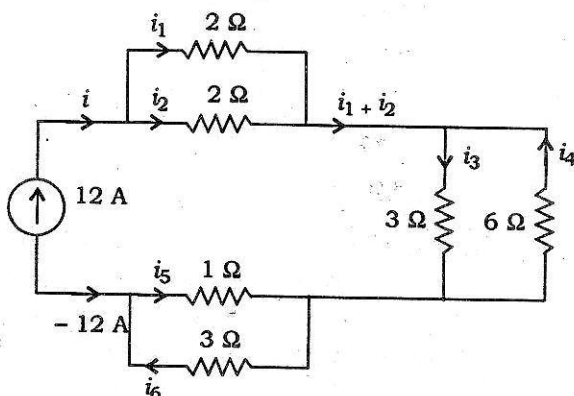


Or

(a) What is lumped circuit? State and explain ladder method of network analysis.

$1 + 3 = 4$


(b) Find  $I_1$ ,  $I_2$  and  $I_3$  using Mesh analysis.

3

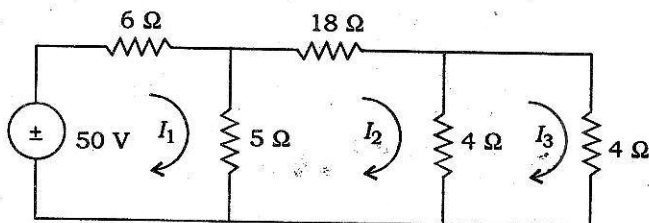

5. (a) State and prove reciprocity theorem. 4

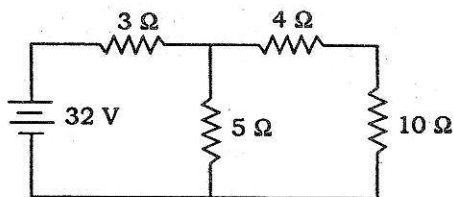
(b) Apply Thevenin's theorem to find current through the  $10\ \Omega$  resistor of the circuit shown in the figure below : 3



Or

(a) State and prove superposition theorem. 4

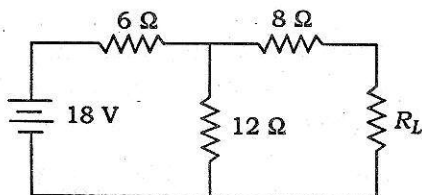(b) In the following circuit, find the value of load resistance  $R_L$  to be connected across terminals  $A$  and  $B$  which would abstract maximum power from the circuit. Also find the value of this maximum power. 3



\*\*\*