

**2 0 2 4**

( NEP-2020 )

( 2nd Semester )

**ELECTRONICS (MAJOR/MINOR)**

**( Basic Semiconductor )**

*Full Marks : 75*

*Time : 3 hours*

*The figures in the margin indicate full marks for the questions*

*Use of Simple Calculator is allowed*

**( SECTION : A—OBJECTIVE )**

( Marks : 10 )

Tick (✓) the correct answer in the brackets provided :

1×10=10

**1.** What happens to the resistance of a pure semiconductor when heated?

- (a) The resistance increases ( )
- (b) The resistance decreases ( )
- (c) The temperature remains the same ( )
- (d) Can't say ( )

**2.** Which of the following is created when trivalent impurities are added to a semiconductor?

- (a) Free electrons ( )
- (b) Valence electrons ( )
- (c) Bound electrons ( )
- (d) Holes ( )

3. What is the random motion of free electrons and holes due to thermal agitation called?
- (a) Pressure ( )
  - (b) Diffusion ( )
  - (c) Ionization ( )
  - (d) Drifting ( )
4. The resistivity of pure silicon is
- (a) 100 cm ( )
  - (b) 6000 cm ( )
  - (c)  $3 \times 10^6$  cm ( )
  - (d)  $6 \times 10^8$  cm ( )
5. Which of the following does the resistivity of a semiconductor depend upon?
- (a) Length of the semiconductor ( )
  - (b) Shape and atomic nature of the semiconductor ( )
  - (c) Atomic nature of the semiconductor ( )
  - (d) Shape of the semiconductor ( )
6. What is the sign of the temperature coefficient of resistance in a semiconductor?
- (a) Negative ( )
  - (b) Positive ( )
  - (c) Zero ( )
  - (d) 1 ( )
7. Schottky diodes are also known as
- (a) PIN diodes ( )
  - (b) Step-recovery diodes ( )
  - (c) tunnel diodes ( )
  - (d) hot-carrier diodes ( )

8. You have an application for a diode to be used in a tuning circuit. A type of diode to be used might be
- (a) an LED ( )
  - (b) a Schottky diode ( )
  - (c) a varactor ( )
  - (d) a Gunn diode ( )
9. The ripple factor of a bridge rectifier is
- (a) 0.482 ( )
  - (b) 0.812 ( )
  - (c) 1.11 ( )
  - (d) 1.21 ( )
10. The PIV of a full-wave center-tapped rectifier circuit is
- (a)  $V$  ( )
  - (b)  $V_m$  ( )
  - (c)  $2 V_m$  ( )
  - (d)  $3$  ( )

**( SECTION : B—SHORT ANSWERS )**

( Marks : 15 )

Answer *five* questions, taking at least *one* from each Unit :

3×5=15

UNIT—I

1. Explain in detail the formation of an *N*-type and a *P*-type semiconductor.
2. Derive the drift and diffusion current in a semiconductor.

UNIT—II

3. Describe how a barrier potential is developed in a junction diode.
4. Explain the concept and formation of Avalanche breakdown in a diode.

UNIT—III

5. Prove that the efficiency of a half-wave rectifier is 40.6%.
6. Explain the various types of filters used in power supplies.

UNIT—IV

7. Explain the construction and working of a tunnel diode.
8. Why is a varactor diode suitable for voltage-controlled tuning?

**( SECTION : C—DESCRIPTIVE )**

( Marks : 50 )

Answer *five* questions, taking at least *one* from each Unit :

10×5=50

UNIT—I

1. Prove that the conductivity of a semiconductor is given by  $e(p_p + n_n)$ .
2. Explain Hall effect. Derive a Hall coefficient. How can Hall effect be used to determine some of the properties of a semiconductor?

UNIT—II

3. Explain how a *p-n* junction works as a diode. Draw and explain its *V-I* characteristics. Discuss the behavior of *p-n* junction when subjected to
  - (a) no bias;
  - (b) forward bias;
  - (c) reverse bias.
4. Draw and describe a full set-up of a power supply system.

### UNIT—III

5. With diagram and relevant waveforms, describe a full-wave and a bridge rectifier. Prove that the ripple factor, of a full-wave centre-tapped rectifier is 0.482.
6. Draw different types of clipper circuits including positive clipper, biased clipper and combination clipper. Give their circuit and explain their operation. Mention how a Zener diode can be configured as a symmetrical shunt clipper.

### UNIT—IV

7. Design a Zener regulator for the following specifications :

Output voltage = 5 V

Load current = 10 mA

Zener wattage = 400 mW

Input voltage = 10 V ± 2 V

8. Write short notes on the following :

$2\frac{1}{2} \times 4 = 10$

(a) PIN diode

(b) Gunn diode

(c) IMPATT diode

(d) Shockley diode

\*\*\*